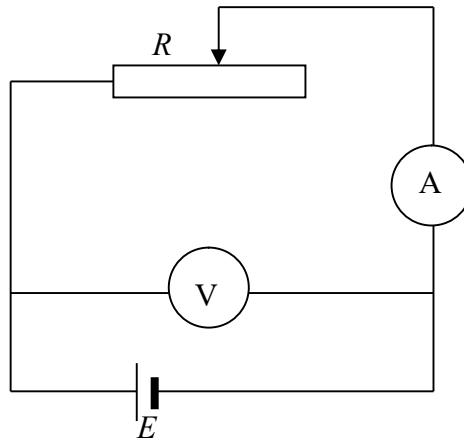


## Experimental problem

The circuit is given in the figure below:




Sliding the contact along the rheostat sets the current  $I$  supplied by the source. For each value of  $I$  the voltage  $U$  across the source terminals is recorded by the voltmeter. The power dissipated in the rheostat is:

$$P = UI$$

provided that the heat losses in the internal resistance of the ammeter are negligible.

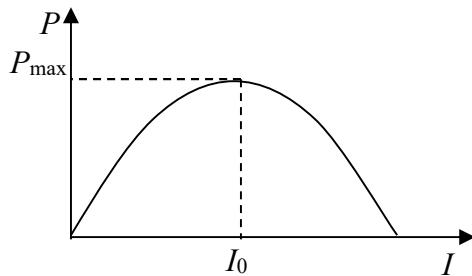1. A typical  $P$ - $I$  curve is shown below:



If the current varies in a sufficiently large interval a maximum power  $P_{\max}$  can be detected at a certain value,  $I_0$ , of  $I$ . Theoretically, the  $P(I)$  dependence is given by:

$$(5.1) \quad P = EI - I^2r,$$

where  $E$  and  $r$  are the EMF and the internal resistance of the dc source respectively. The maximum value of  $P$  therefore is:

$$(5.2) \quad P_{\max} = \frac{E^2}{4r},$$

and corresponds to a current:

$$(5.3) \quad I_0 = \frac{E}{2r}.$$

2. The internal resistance is determined through (5.2) and (5.3) by recording  $P_{\max}$  and  $I_0$  from the experimental plot:

$$r = \frac{P_{\max}}{I_0^2} .$$

3. Similarly, EMF is calculated as:

$$E = \frac{2P_{\max}}{I_0}.$$

4. The current depends on the resistance of the rheostat as:

$$I = \frac{E}{R+r}.$$


Therefore a value of  $R$  can be calculated for each value of  $I$ :

$$(5.4) \quad R = \frac{E}{I} - r.$$

The power dissipated in the rheostat is given in terms of  $R$  respectively by:

$$(5.5) \quad P = \frac{E^2 R}{(R+r)^2}.$$


The  $P$ - $R$  plot is given below:

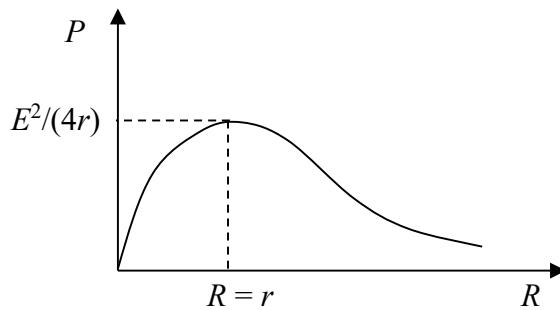

Its maximum is obtained at  $R = r$ .

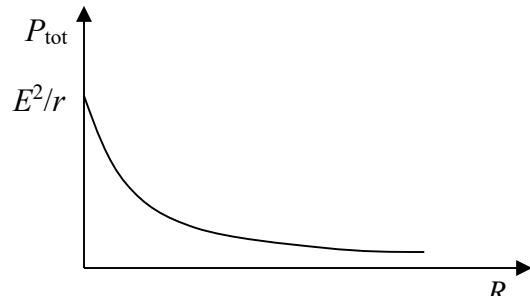5. The total power supplied by the dc source is:

$$(5.6) \quad P_{\text{tot}} = \frac{E^2}{R+r}.$$



6. The efficiency respectively is:

$$(5.7) \quad \eta = \frac{P}{P_{\text{tot}}} = \frac{R}{R+r}.$$

