
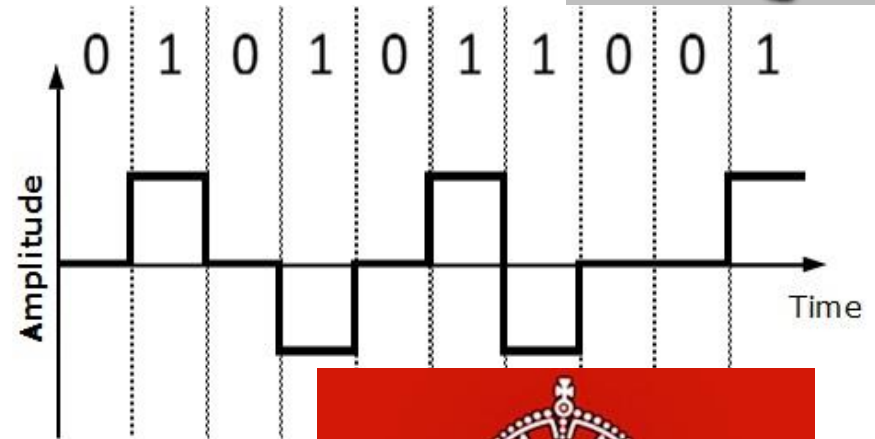


Proiectare Logica

Digital Logic Design


Lab 03

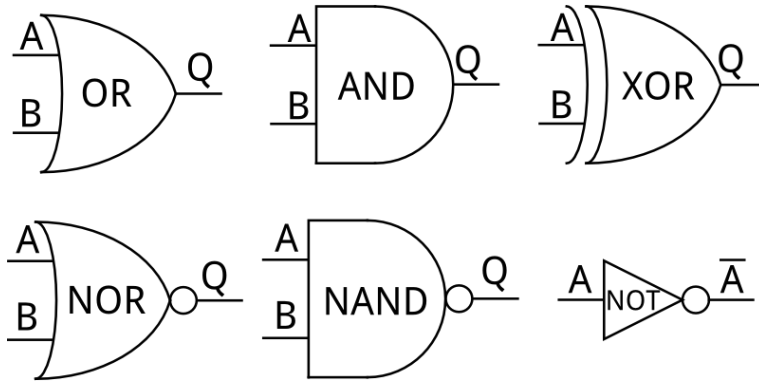

Verificarea identitatilor

Folosind :

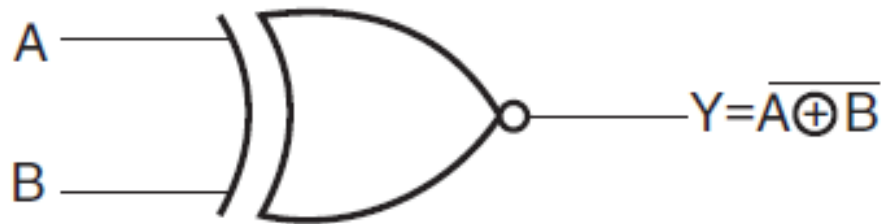- tabele de adevar
- diagrame Venn
- wronex si poarta XNOR (coincidenta)
- regulile algebrei booleene
- forme canonice : sume de produse; produse de sume




$$Y = (\overline{A \oplus B}) = (A.B + \overline{A}.\overline{B})$$


A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

Demonstrati identitatile: tabele adev

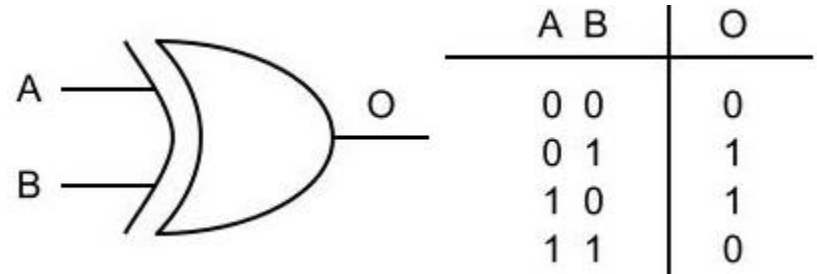- $(A + B)(A + C) = A + BC$
- $A \oplus B = A'B + AB'$ XOR $\equiv$ Suma mod 2
- $(A \oplus B)' = AB + A'B'$
- $A \oplus B \oplus AB = A + B$
- $A(B \oplus C) = AB \oplus AC$



Poarta XNOR $\equiv$ Coincidenta

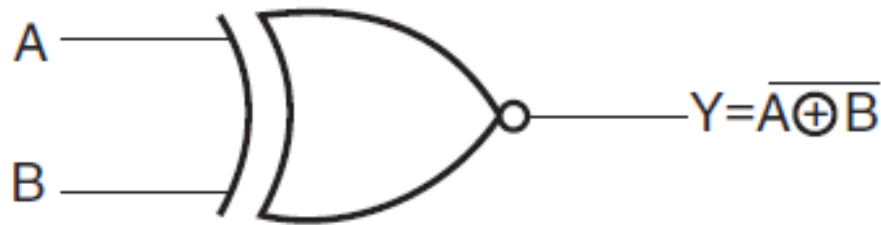

$$Y = \overline{(A \oplus B)} = (A.B + \overline{A}.\overline{B})$$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1


Verificati identitatile folosind tabele de adevar

- 1. $(A + B)(A + C) = A + BC$**
- 2. $A \oplus B = A'B + AB'$**
- 3. $(A \oplus B)' = AB + A'B'$**
- 4. $A \oplus B \oplus AB = A + B$**
- 5. $A(B \oplus C) = AB \oplus AC$**
- 6. $(A \oplus B)' = (A' + B) \cdot (A + B')$**

Verificarea identitatii

$$A \oplus B \oplus AB = A + B$$

folosind wronex

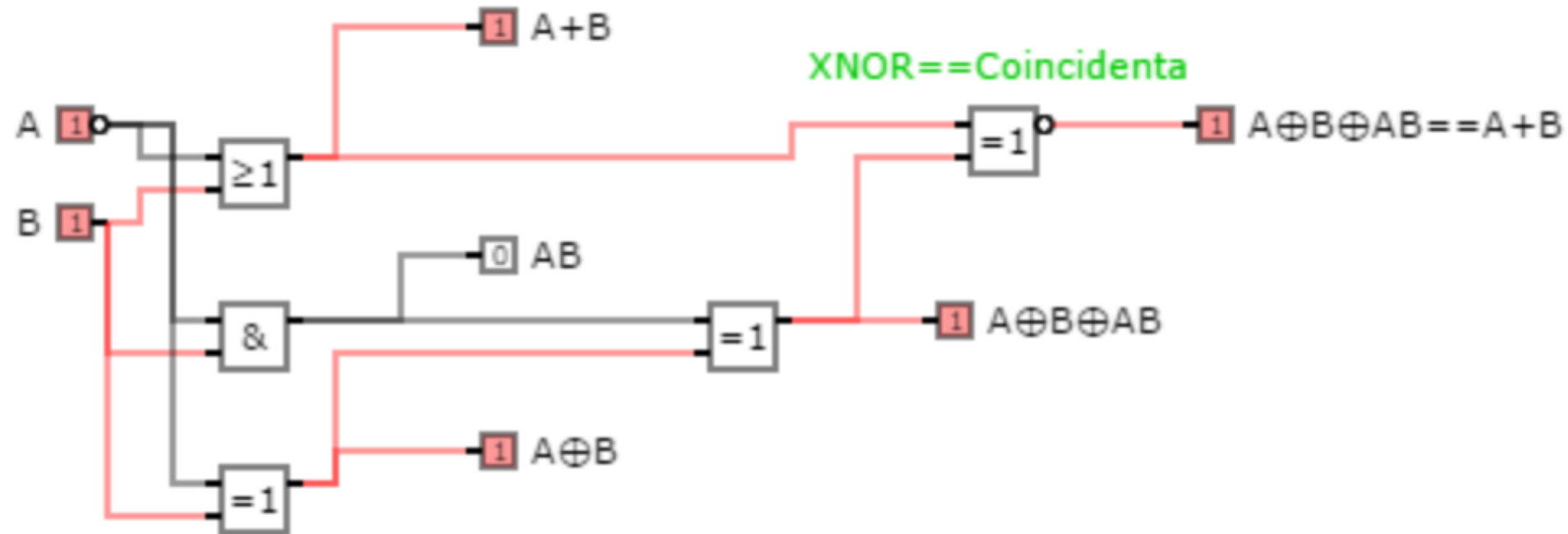

Demonstrati folosind wronex

- $A \oplus B = \bar{A}B + A\bar{B}$.
- $(A \oplus B)' = AB + A'B'$

Forme canonice: exemplu

- Fie functia f definita de tabelul:

i	A	B	C	f	mintermeni (m_i)	Maxtermeni (M_i)
0	0	0	0	1	$A'B'C'$	$A+B+C$
1	0	0	1	0	$A'B'C$	$A+B+C'$
2	0	1	0	0	$A'BC'$	$A+B'+C$
3	0	1	1	1	$A'BC$	$A+B'+C'$
4	1	0	0	1	$AB'C'$	$A'+B+C$
5	1	0	1	0	$AB'C$	$A'+B+C'$
6	1	1	0	1	ABC'	$A'+B'+C$
7	1	1	1	1	ABC	$A'+B'+C'$

FCD: $f = A'B'C' + A'BC + AB'C' + ABC' + ABC = \sum m(0, 3, 4, 6, 7)$

FCD= Forma Canonica Disjunctiva (foloseste operatia disjunctiva "+")

FCC: $f = (A + B + C') \cdot (A + B' + C) \cdot (A' + B + C') = \prod M(1, 2, 5)$

FCC= Forma Canonica Conjunctiva (foloseste operatia conjunctiva ".")

$f' = A'B'C + A'BC' + AB'C \Rightarrow f = (f')' = (A'B'C)'(A'BC')'(AB'C)'$

Tema

- Sa se gaseasca mintermenii si maxtermenii functiei

i	A	B	C	f	mintermeni (m_i)	Maxtermeni (M_i)
0	0	0	0	0	$A'B'C'$	$A+B+C$
1	0	0	1	1	$A'B'C$	$A+B+C'$
2	0	1	0	0	$A'BC'$	$A+B'+C$
3	0	1	1	0	$A'BC$	$A+B'+C'$
4	1	0	0	1	$AB'C'$	$A'+B+C$
5	1	0	1	1	$AB'C$	$A'+B+C'$
6	1	1	0	1	ABC'	$A'+B'+C$
7	1	1	1	0	ABC	$A'+B'+C'$

FCC si FCD

- Scrieti FCD si FCC pentru functiile si precizati mintermenii si maxtermenii.

Tabela de adevar

A	B	C	F (ABC)
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

Tabela de adevar

A	B	C	F (ABC)
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0

- 01101101; 10010101; 11111011; etc

Diagramme Venn

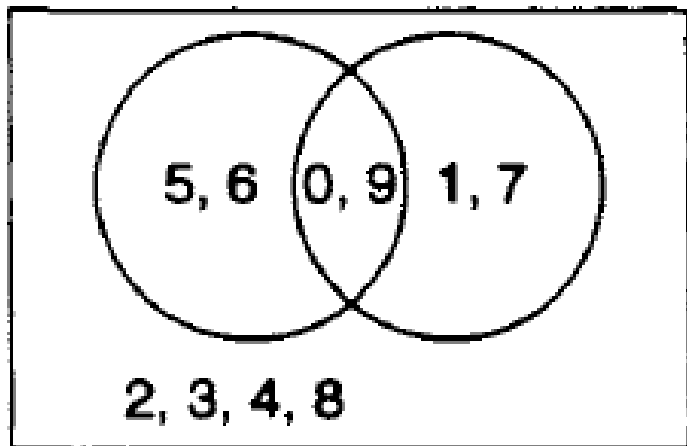


Diagrama in teoria multimilor



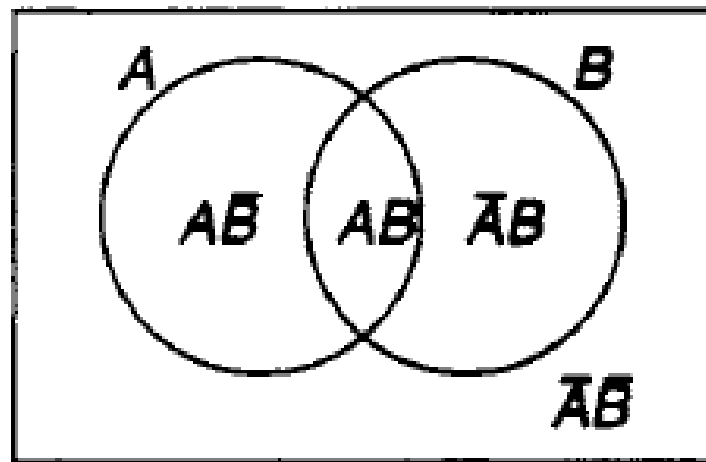



Diagrama Venn

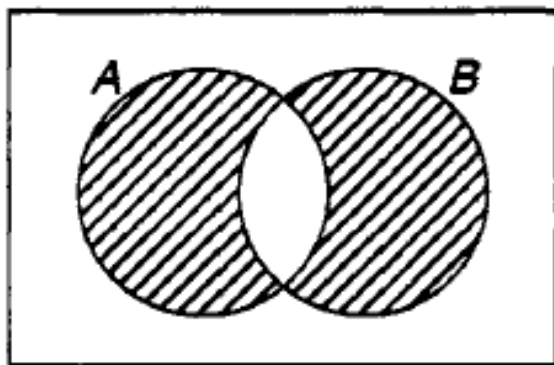

$$A\bar{B} + \bar{A}B$$

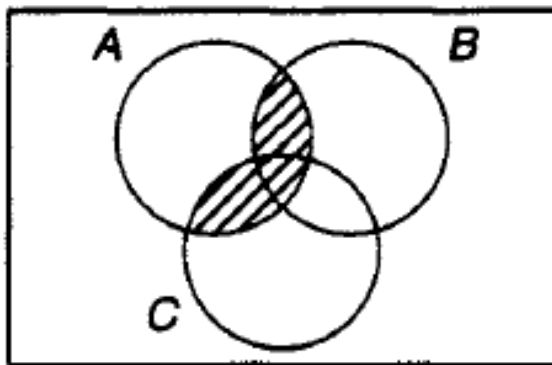

$$AB + AC$$

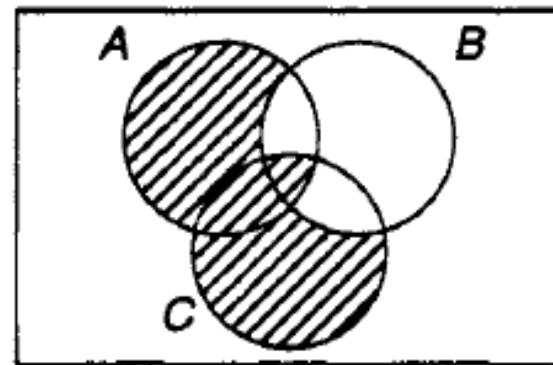

$$AC + BC + AB$$


Diagramme Venn: rappresentari canonice

- 2 variabile

$f(A, B)$	$\bar{A}$	A
$\bar{B}$	$\bar{A}\bar{B}$	$A\bar{B}$
B	$\bar{A}B$	AB

$A \oplus B$	$A = 0$	$A = 1$
$B = 0$	0	1
$B = 1$	1	0
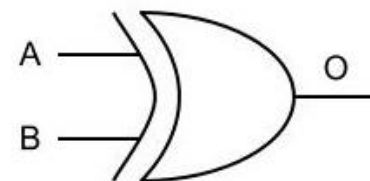
$$f(A, B) = A \oplus B = A\bar{B} + \bar{A}B$$



A	B	O
0	0	0
0	1	1
1	0	1
1	1	0

Diagramme Veitch asociate

- 3 variabile

	$\bar{A}$		A	
$f(A, B, C)$	$\bar{A}\bar{B}$	$\bar{A}B$	AB	$A\bar{B}$
$\bar{C}$	$\bar{A}\bar{B}\bar{C}$	$\bar{A}B\bar{C}$	$AB\bar{C}$	$A\bar{B}\bar{C}$
C	$\bar{A}\bar{B}C$	$\bar{A}BC$	ABC	$A\bar{B}C$
	$\bar{B}$		B	
	$\bar{B}$		B	

$\bar{C}$
 C

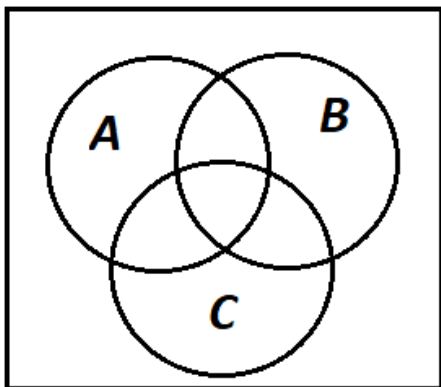


Diagramme Venn - Veitch


- 3 variable

	$\bar{A}$		A	
$f(A, B, C)$	$\bar{A}\bar{B}$	$\bar{A}B$	AB	$A\bar{B}$
$\bar{C}$	$\bar{A}\bar{B}\bar{C}$	$\bar{A}B\bar{C}$	$AB\bar{C}$	$A\bar{B}\bar{C}$
C	$\bar{A}\bar{B}C$	$\bar{A}BC$	ABC	$A\bar{B}C$

$\bar{C}$
 C

Diagrama
Veitch

$f(A, B, C)$	$\bar{A}\bar{B}$	$\bar{A}B$	AB	$A\bar{B}$
$\bar{C}$	1	1	1	1
C	0	1	1	0

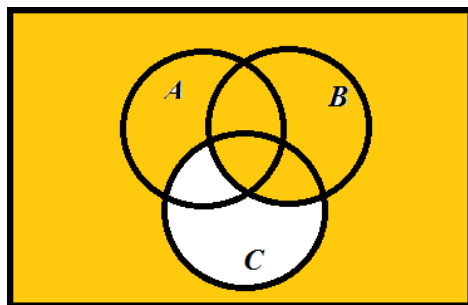


$$f(A, B, C) = B + \bar{C}$$

Diagrama Venn

Diagrama Venn de 4 variabile

- Este corecta diagrama Venn de mai jos?

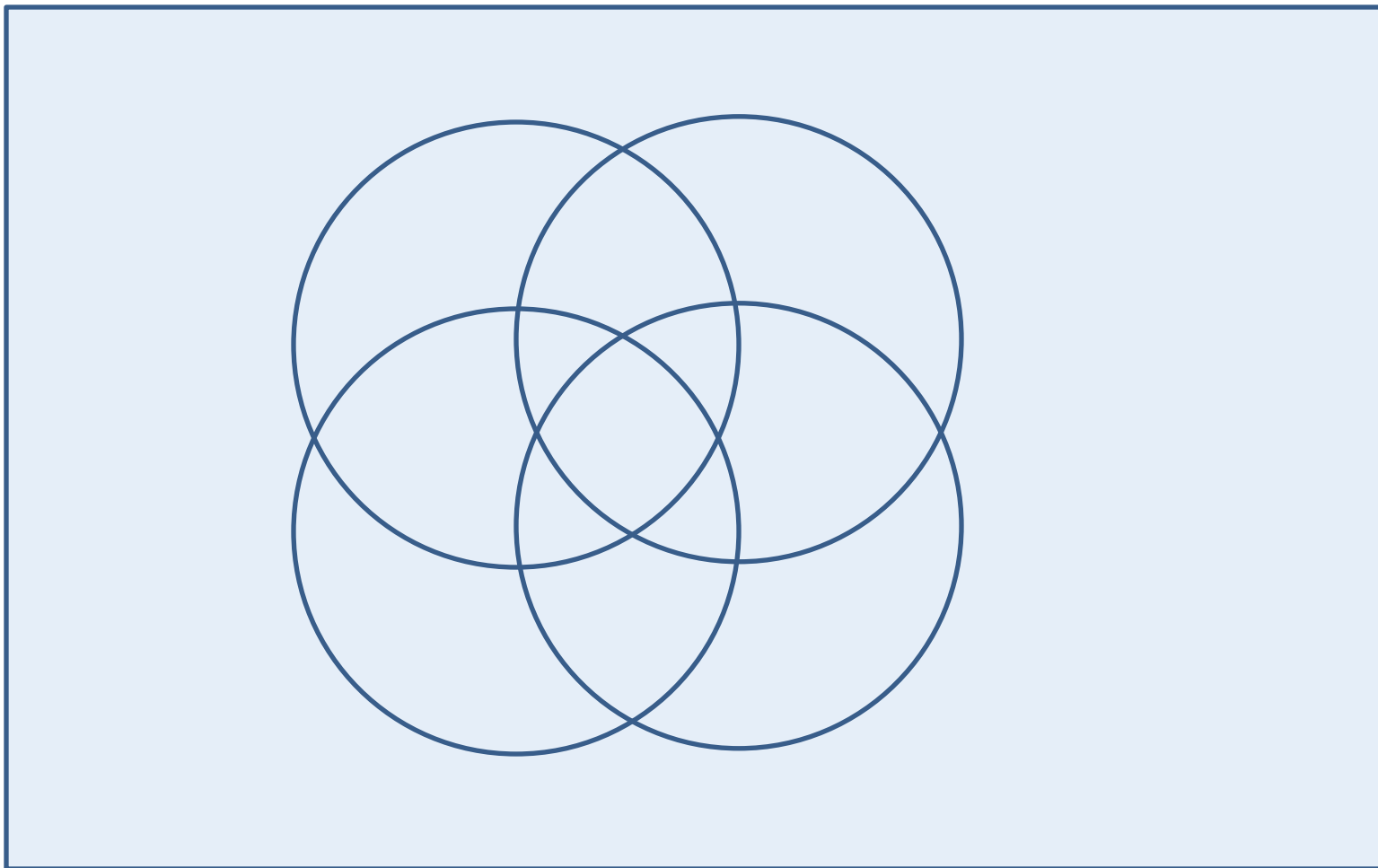


- Cate multimi disjuncte are aceasta diagrama?

Diagramme Veitch: reprezentari canonice

- 4 variabile

		$\bar{A}$		A	
	$f(A, B, C, D)$	$\bar{A}\bar{B}$	$\bar{A}B$	AB	$A\bar{B}$
$\bar{D}$	$\bar{C}\bar{D}$	$\bar{A}\bar{B}\bar{C}\bar{D}$	$\bar{A}B\bar{C}\bar{D}$	$AB\bar{C}\bar{D}$	$A\bar{B}\bar{C}\bar{D}$
D	$\bar{C}D$	$\bar{A}\bar{B}C\bar{D}$	$\bar{A}BC\bar{D}$	$ABC\bar{D}$	$A\bar{B}C\bar{D}$
$\bar{D}$	$C\bar{D}$	$\bar{A}\bar{B}C\bar{D}$	$\bar{A}BC\bar{D}$	$ABC\bar{D}$	$A\bar{B}C\bar{D}$
		$\bar{B}$		B	
		$\bar{C}$		C	

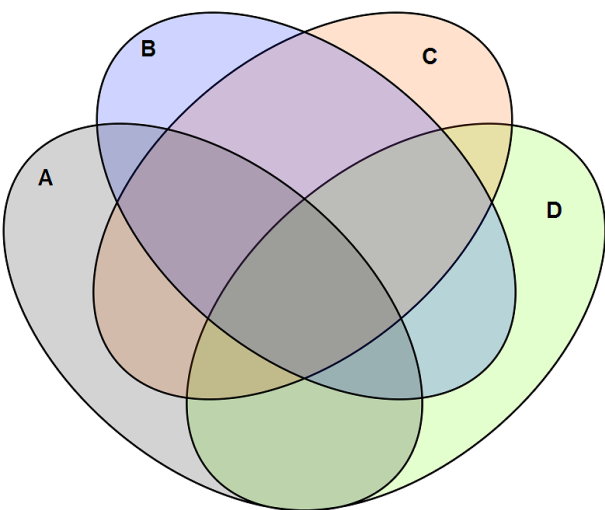

**Diagrama Venn
Corecta**

